

EE335 Electronics
FINAL Exam, June 1, 2018

Name, Surname:
Instructor: R. Kopru

Student No:

Q1. (18) For the DC analysis of a BJT amplifier seen in Fig. 1, determine the followings:

- a) (4) I_{BQ}
- b) (6) I_{CQ}, V_{CEQ}
- c) (2) operating point Q
- d) (6) V_E, V_C, V_B .

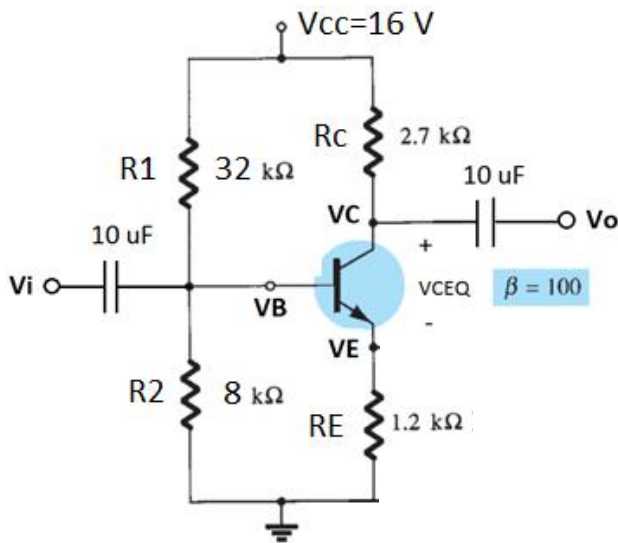


Fig. 1.

Q2. (22) Consider again the same BJT amplifier of Fig. 1.
For the AC analysis, determine the followings:

- a) (03) r_e .
- b) (04) calculate Z_i and Z_o .
- c) (08) derive the expression of A_v
- d) (03) calculate the value of A_v .
- e) (04) Write the output voltage expression $v_o(t)$ if the input voltage is $v_i(t) = 10 \sin(2\pi 1000t), mV$.

SOLUTIONS


Q1. We have $V_{BE}=0.7\text{ V}$, $V_{CC}=16\text{ V}$, $R_1=32.0\text{ k}$, $R_2=8.0\text{ k}$, $R_E=1.2\text{ k}$, $R_C=2.7\text{ k}$, $\beta = 100$.

a) DC ANALYSIS:

The DC analysis of this **"UNbypassed amplifier is exactly the SAME AS the bypassed case"** worked in the document **"BJT AMP bypassed"** (see courseonline), therefore here we write everything as the same from that document.

We should draw the DC eqvn. circuit. For this; we do the following:

- all caps. should be "open-circuited".

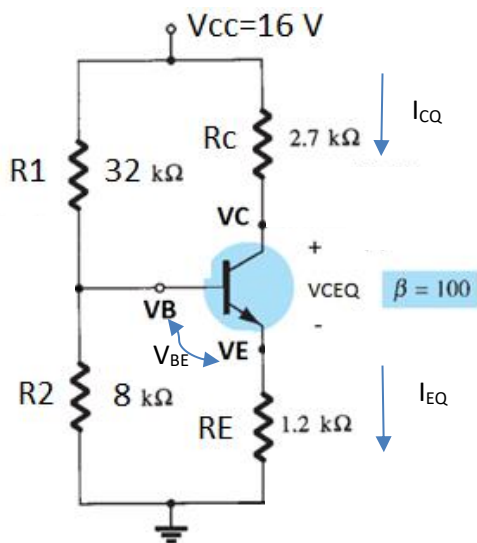


DC. eqvn. circuit.

Using Thevenin's method we have,

$$R_{TH} = R_1 || R_2 = R_1 * R_2 / (R_1 + R_2) = 6.4\text{ k}$$

$$E_{TH} = V_{CC} * R_2 / (R_1 + R_2) = 3.2\text{ V}$$
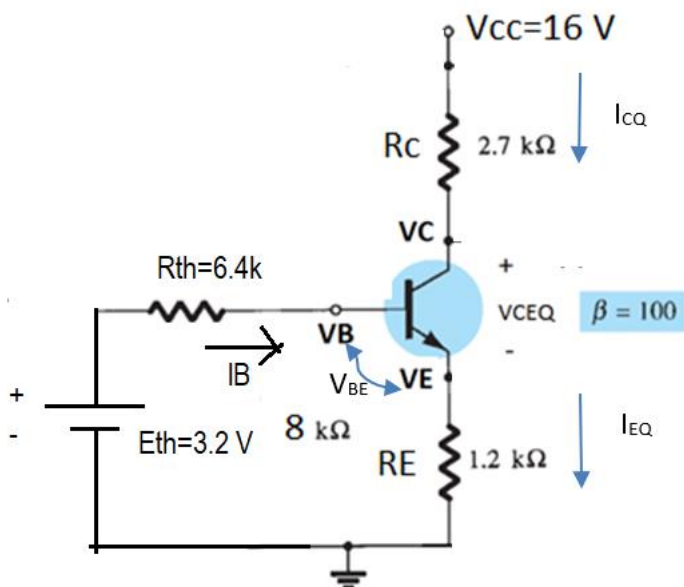
$$I_{BQ} = (E_{TH} - V_{BE}) / (R_{TH} + (\beta + 1) * R_E) = 0.0196\text{ mA} = 19.6\text{ μA}$$



b)
 $I_{CQ} = \beta \cdot I_B = 1.9592 \text{ mA}$
 $I_{EQ} = (\beta + 1) \cdot I_B = 1.9788 \text{ mA}$
 KVL for the output: $V_{CC} = I_C \cdot R_C + V_{CE} + I_E \cdot R_E$, so we have $V_{CEQ} = V_{CC} - I_C \cdot R_C - I_E \cdot R_E = 8.3354 \text{ V}$

c) $Q(V_{CEQ}, I_{CQ}) = Q(8.3354 \text{ V}, 1.9592 \text{ mA})$

d)
 $V_E = I_E \cdot R_E = 2.3746 \text{ V}$
 Since $V_{CE} = V_C - V_E$, so we have $V_C = V_{CE} + V_E = 10.71 \text{ V}$
 Since $V_{BE} = V_B - V_E$, so we have $V_B = V_{BE} + V_E = 3.0746 \text{ V}$

Q2.

a) $r_e = V_T / I_{EQ} = 26 \text{ mV} / 1.9788 \text{ mA} = 13.1 \Omega = 0.0131 \text{ k}\Omega$.

b) **AC ANALYSIS:**


The AC analysis of this **“UNbypassed amplifier is DIFFERENT FROM the bypassed case”** worked in the document **“BJT AMP bypassed”** (see courseonline), therefore we do the followings:

The AC equivalent circuit is to be drawn. For this, we need to make the followings:

- All caps. are to be “short-circuited”.
- Supply source is to be grounded.


The resulting circuit would be as follows:

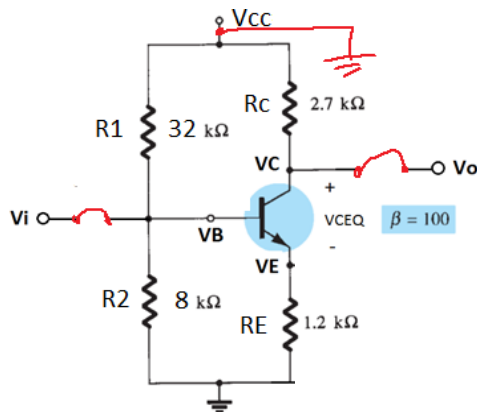NOTICE that here, R_E is NOT BYPASSED since it does not have any CE bypass cap. across it.



If the transistor in the above circuit is replaced by its **AC eqvn. circuit** and the circuit is rearranged, the **“complete AC eqvn. circuit of the BJT amplifier”** would be as follows

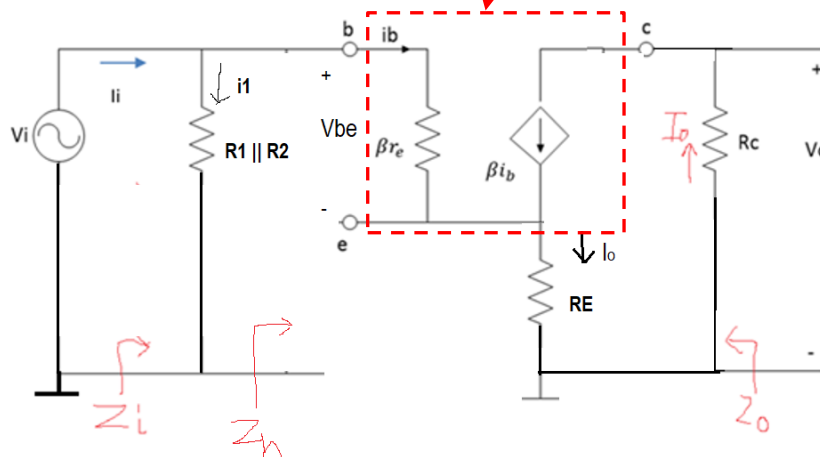- 1) **IMPORTANT: r_o is IGNORED, i.e. $r_o \rightarrow \infty$**
- 2) **NOTE: YOU ARE RESPONSIBLE TO DRAW THIS AC EQVN. CIRCUIT WITH ONLY $r_o \rightarrow \infty$ IN THE FINAL EXAM.**



FINDING INPUT IMPEDANCE (Zi): from the AC eqvn. circuit above, we write;

$$Z_i = V_i / I_i = R_1 \parallel R_2 \parallel Z_b$$

where $Z_b = V_b / i_b$ with $V_b = V_{be} + V_{RE} = (\beta r_e) i_b + i_o R_E$. Notice that here $V_{be} = (\beta r_e) i_b$ and $V_{RE} = i_o R_E$. Also it is easy to see that $i_o = i_b + \beta i_b = (\beta + 1) i_b$, therefore we have

$$V_b = (\beta r_e) i_b + (\beta + 1) i_b R_E$$

If we assume that $\beta + 1 \cong \beta$ then we can rewrite the equation above as follows

$$V_b \cong (\beta r_e) i_b + \beta i_b R_E$$

$$\boxed{V_b = \beta i_b (r_e + R_E)}$$

Inserting this into the above expression of $Z_b = V_b / i_b$, we would have

$$Z_b = \frac{V_b}{i_b} = \frac{\beta \cancel{i_b} (r_e + R_E)}{\cancel{i_b}} = \beta (r_e + R_E)$$

which yields the input impedance as

$$Z_i = V_i / I_i = R_1 \parallel R_2 \parallel Z_b$$

$$Z_i = R_1 \parallel R_2 \parallel \beta (r_e + R_E)$$

or

$$Z_i = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{\beta (r_e + R_E)} \right)^{-1}$$

Putting the numerical value into Z_i expression we write

$$Z_i = \left(\frac{1}{32} + \frac{1}{8} + \frac{1}{100(0.0131 + 1.2)} \right)^{-1}$$

(Note: since we know the result will be in $k\Omega$, we do not put

“k” near 32, 8, 0.0131 and 1.2).

$$= \left(0.0313 + 0.125 + \frac{1}{100(1.2131)} \right)^{-1}$$


$$= \left(0.0313 + 0.125 + \frac{1}{121.31} \right)^{-1}$$

$$= (0.0313 + 0.125 + 0.0082)^{-1}$$

$$= (0.1645)^{-1}$$


$$Z_i = 6.079 \text{ } k\Omega$$

FINDING OUTPUT IMPEDANCE (Z_o): $Z_o = \frac{v_o}{i_o} |_{V_i \rightarrow 0}$. This expression tells us, first V_i input voltage must be set to zero volt (i.e. it should be connected to ground.) therefore, the circuit can further be drawn as follows to find Z_o . Notice that since V_i is grounded (i.e. $V_i \rightarrow 0$ V), V_b also becomes 0 V. Then, since $V_b=0$ V, i_b will be zero. Therefore the current source of βi_b has become zero amper source which means that it can be assumed as “open” (see the figure below).

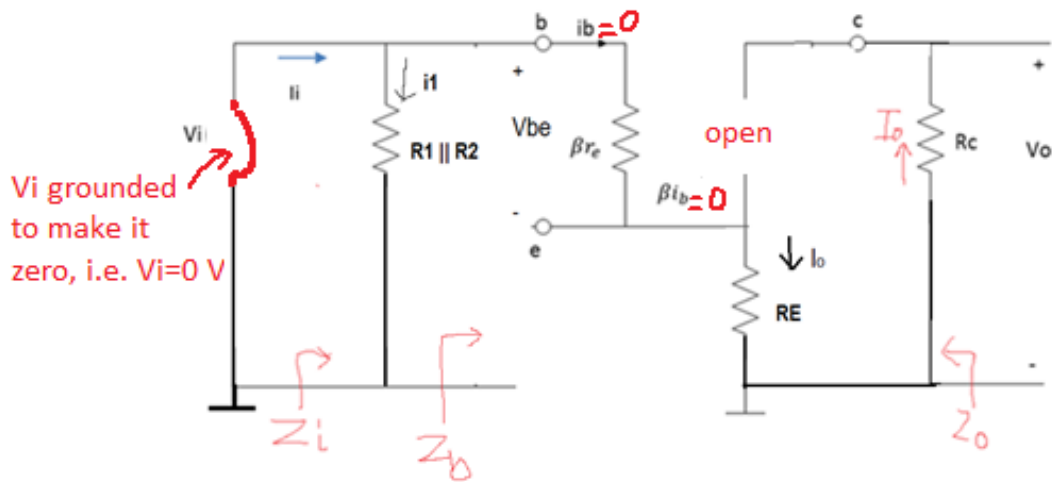

And now, seeing $Z_o=R_c=2.7 \text{ k}\Omega$ is really very easy !

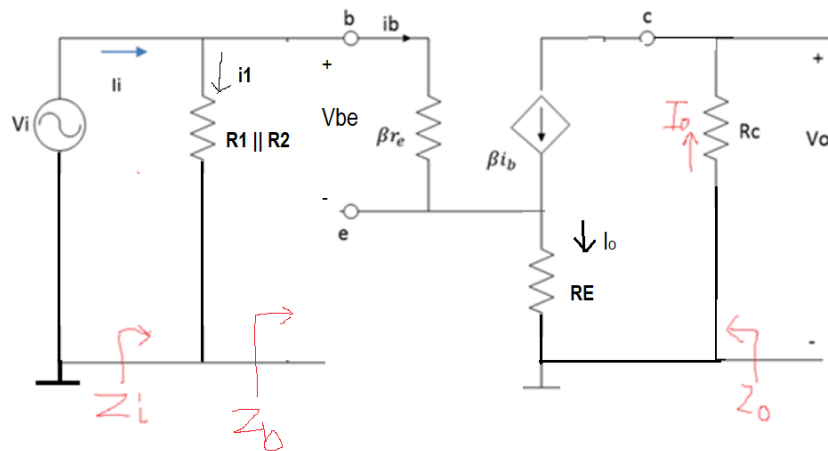FINDING AC VOLTAGE GAIN (A_v): Let us redraw the “complete AC eqvn. circuit of the BJT amplifier” drawn in part b as seen in the following:



The AC voltage gain is given by

$$A_v = \frac{v_o}{v_i}$$

where from the examining the circuit above we see that the output AC voltage can be written as

$$v_o = -i_o R_c$$

if we remember again we know that $i_o = i_b + \beta i_b = (\beta + 1)i_b$

$$v_o = -(\beta + 1)i_b R_c$$

Again if we assume that $\beta + 1 \cong \beta$, we write

$$v_o \cong -\beta i_b R_c$$

If we look at the circuit, we can see that the input voltage v_i is equal to the voltage V_b at the base (b) terminal of the transistor; and we can write it as

$$v_i = v_b$$

where we see from the circuit that $v_b = v_{be} + v_{RE}$. We can also see from the circuit that $v_{be} = (\beta r_e)i_b$ and $v_{RE} = R_E(\beta + 1)i_b$. Thus,

$$v_i = v_b$$

$$v_i = (\beta r_e)i_b + R_E(\beta + 1)i_b$$

Again since we assume that $\beta + 1 \cong \beta$, we write

$$v_i \cong \beta i_b (r_e + R_E)$$

As a conclusion we write

$$A_v = \frac{v_o}{v_i} = \frac{-\cancel{\beta} i_b R_c}{\cancel{\beta} i_b (r_e + R_E)}$$

$$A_v = \frac{v_o}{v_i} = \frac{-R_c}{(r_e + R_E)}$$

d)

Putting the numerical value into A_v expression we write

$$A_v = \frac{v_o}{v_i} = - \frac{(2.7 \text{ k}\Omega)}{(0.0131 \text{ k}\Omega + 1.2 \text{ k}\Omega)}$$

$$= - \frac{2.7 \text{ k}\Omega}{1.2131 \text{ k}\Omega}$$

$$= - \frac{2700 \text{ }\Omega}{1213.1 \text{ }\Omega}$$

$$A_v = \frac{v_o}{v_i} = -2.1932$$

e)

$$v_o = A_v v_i = (-2.1932)(10 \sin(2\pi 1000t), \text{ mV}) = -21.932 \sin(2\pi 1000t), \text{ mV}$$